




4N35



by primerobotics

The 4N35 is an optocoupler that consists of a gallium arsenide infrared LED and a silicon NPN phototransistor. When the input signal is applied to the LED in the input terminal, the LED lights up. After receiving the light signal, the light receiver then converts it into electrical signal and outputs the signal directly or after amplifying it into a standard digital

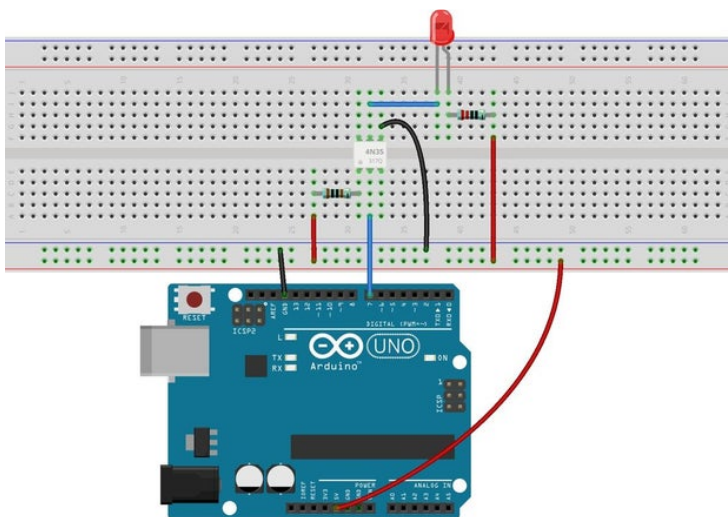level. Thus, the transition and transmission of electricity-light-electricity is completed. Since light is the media of the transmission, meaning the input terminal and the output one are isolated electrically, this process is also be known as electrical isolation.



fritzing

Step 1: Components

- Arduino Uno board * 1
- Resistor (1k \blacksquare) * 1
- USB cable * 1
- Breadboard * 1
- 4N35 * 1
- Jumper wires
- Resistor (220 \blacksquare) * 1


Step 2: Principle:

The 4N35 is an optocoupler for general purpose application. It consists of gallium arsenide infrared LED and a silicon NPN phototransistor.

What an optocoupler does is to break the connection between signal source and signal receiver, so as to stop electrical interference. In other words, it is used to prevent interference from external electrical signals. 4N35 can be used in AV conversion audio circuits. Broadly it is widely used in electrical isolation for a general optocoupler.

See the internal structure of the 4N35 above. Pin 1 and 2 are connected to an infrared LED. When the LED is electrified, it'll emit infrared rays. To protect the LED from burning, usually a resistor (about 1K) is connected to pin 1. Then the NPN phototransistor is power on when receiving the rays. This can be done to control the load connected to the phototransistor. Even when the load short circuit occurs, it won't affect the control board, thus realizing good electrical isolation.

Step 3: The Schematic Diagram:

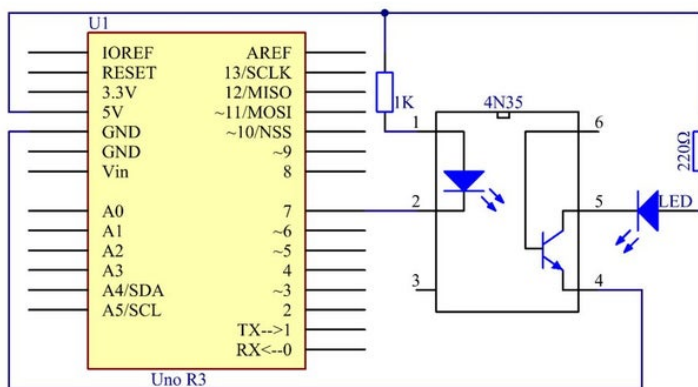

Step 4: Procedures:

In this experiment, use an LED as the load connected to the NPN phototransistor. Connect pin 2 of the 4N35 to pin 7 of the control board, and pin 1 to a 1K current limiting resistor and then to 5V. Connect pin 4 to GND of the Uno, and pin 5 to the cathode of the LED. Then hook the anode of the LED to 5V after connecting with a 220 Ohm resistor. When in program, a LOW level is given to pin 7, the infrared LED will emit infrared rays. Then the phototransistor receives infrared rays and gets electrified, and the LED cathode is LOW, thus turning on the LED. Also

Step 3:

Upload the sketch to the Arduino Uno board

Click the Upload icon to upload the code to the control board.

you can control the LED by circuits only – connect pin 2 to ground and it will brighten

Step 1:

Build the circuit.

Step 2:

Download the code from
<https://github.com/primerobotics/Arduino>

If "Done uploading" appears at the bottom of the window, it means the sketch has been successfully uploaded.

Step 5: Code

```
//Turn on a led by
4n35

//turn on the LED
for half a second,then off for half a second,repeatedly

//info@primerobotics.in

//www.primerobotics.in

int OptoPin=7;
//attach the input of the 4n35 to pin 7

void setup()
{

  pinMode(OptoPin, OUTPUT); //set it as OUTPUT

}

void loop()
{


  digitalWrite(OptoPin, LOW); //set the OptoPin as LOW level,then the led
connected on the output of 4n35 will be light

  delay(500);
//delay 500ms

  digitalWrite(OptoPin, HIGH); //turn off the led

  delay(500);
//delay 500ms

}
```

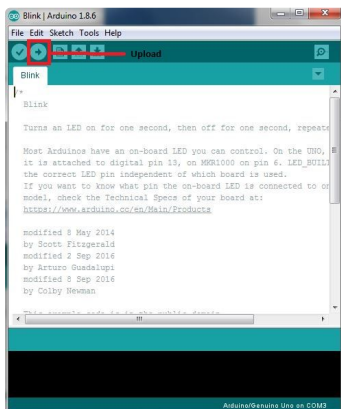

Code Analysis

```
void loop()
{
  digitalWrite(OptoPin, LOW);
  delay(500); //delay 500ms
  digitalWrite(OptoPin, HIGH);
  delay(500); //delay 500ms
}
```

The code in this experiment is very easy to understand. Set pin 7 as Low level and the LED will light up; set it as High, and the LED goes out.



You should add "optocoupler" and/or the word "tutorial" to the title to make it easier for people to find.