



ROBOT



Brandon · Aug 17 · 5 min read



Controlling a DC Brushed Motor with the L298N Motor Controller

I've recently noticed the same inexpensive gear motor being sold by many different sellers on Amazon and on individual store fronts.



In this example, I demonstrate how to control a fairly common 6V gear motor with the L298N Motor Controller.


[Guides](#) · [Introduction to Arduino](#)

33 views 0 comments





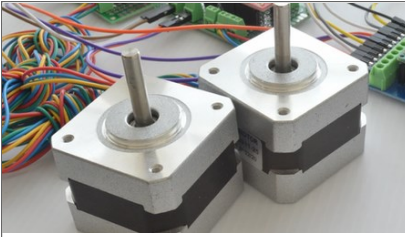
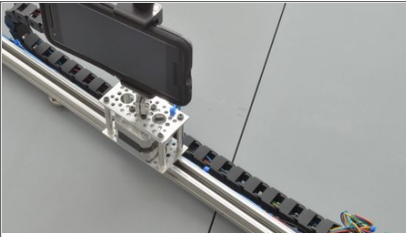
Recent Posts

[See All](#)






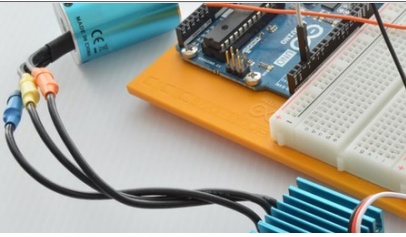
Simultaneously Controlling Stepper Motors ... Arduino

 648  0 






DIY Arduino Camera Phone Slider

 95  0 2 



Controlling a Brushless Motor with Arduino

 710  0 3 

Parts Needed:

In this example, I used the following parts:

- [Arduino Uno](#)

- [Breadboard](#)



[Male to male jumper wire](#)

[Write a comment...](#)

- [Brushed DC Motor Kit](#)

- Male to female jumper wire
- DC brushed gear motor
- Dual L298N motor controller
- [Potentiometer](#)
- [6V](#) and [12V](#) AA battery holder

The L298N Motor Controller

About

Terms and Conditions


Privacy Policy

L298N actually refers to a specific chip that is ultimately responsible for driving the motors. While it is possible to run a motor with only the chip, it's often mounted to a printed circuit board and heat sink. The board includes header pins and terminal blocks to make the power and communication connections more convenient.


The board used in this example has a combination of screw terminal blocks and male header pins. The two sets of screw terminals are on opposite sides of the board, and connected to the leads of the motors. The screw terminal blocks on the bottom of the board are related to power. The left connection is for the input voltage; this board can be powered by up to 12V. The center screw terminal connection is for ground and the right connection provides a 5V output voltage jumper will disable the 5V supply.

Never miss a post. Enter your email here*

Subscribe

 

The set of header pins, on the bottom of the board, control the speed and direction of the motors. The ENA, IN1, and IN2 pins are directly related to the speed and direction of the left motor outputs. The ENB, IN3, and IN4 pins control the speed and direction of the right motor outputs. For the left motor, sending a signal between 0-5V to the ENA will control the speed of the motor. A value of 5V will cause the motor to move at full speed and a value of 0V will stop the motor. Some boards come with a jumper connected to the ENA and ENB pins. This connects 5V to these pins so the motors will always move at full speed. Remove these jumpers to control the speeds of the motors. The IN1 and IN2 pins should be set to HIGH or LOW. For example, if IN1 receives a HIGH signal, then IN2 must receive a LOW signal. Reversing this changes the direction of the motor. These methods also apply to the other motor output with the ENB, IN3, and IN4 pins.

 


Motor Speed

Motor Direction

Building the Circuit

For this example, I used a potentiometer with an Arduino Uno to control the speed of the motor. To build this circuit:

- connect 5V and GND from the Arduino to the breadboard
- place the potentiometer over the center of the breadboard.
- connect the potentiometer to 5V, GND, and A0
- connect pin 3 on the Arduino to ENA
- connect pin 4 to IN1
- connect pin 5 to IN2
- connect the motor leads to the motor output screw terminals on the left side of the board
- Connect the power source to the board with the switch turned off. To start, I will use a 6V AA battery holder (4 batteries). Later in the example, I will use a 12V AA battery holder (8 batteries).

 

Arduino Code

I want to set up the Arduino code so that rotating the potentiometer directly controls the speed and direction of a single motor. I also want it so that the midpoint of the potentiometer will stop the motor, moving the potentiometer. Let's first start the code by defining the pins. I will use pin A0 to read the potentiometer value, and pins 3-5 for the ENA, IN1, and IN2 pins respectively. I also define integer variables for the value that is being read from the potentiometer and for the motor speed.

```
#define PotPin A0
#define ENAPin 3
#define IN1Pin 4
#define IN2Pin 5
```

```
int PotVal;
int MotorSpeed;
```

In the setup, pins 3-5 should be set to outputs and the baud rate can be set to 9600.

```
void setup() {
  pinMode(ENAPin, OUTPUT);
  pinMode(IN1Pin, OUTPUT);
  pinMode(IN2Pin, OUTPUT);
  Serial.begin(9600);
}
```

In the loop, use the "analogRead" command to read the value from the potentiometer and save it to a

variable. This value should be in between 0 and 1023, so the midpoint could be rounded to 512.

```
PotVal = analogRead(PotPin);
```

I can use an "if/else" statement to control the speed and direction of the motor, based on what's being read from the potentiometer. If the potentiometer value is greater than or equal to 512, then I'll use the "digitalWrite" command to set IN1 to HIGH and IN2 to LOW. Since I plan on using the "analogWrite" command to control the speed of the motor, I need to map the potentiometer value. This value should be mapped from 512-1023 to 0-255. I also use print statements to help with debugging in the future.

```
if (PotVal >= 512){
  digitalWrite(IN1Pin, HIGH);
  digitalWrite(IN2Pin, LOW);
  MotorSpeed = map(PotVal, 512, 1023, 0, 255);
  analogWrite(ENA1Pin, MotorSpeed);


  Serial.print("Pot Value: ");
  Serial.print(PotVal);
  Serial.print(" ");
  Serial.print("Forward Motor Speed: ");
  Serial.println(MotorSpeed);
}
```

To make the motor go in the other direction, I'll need to reverse the signals going to the IN1 and IN2 pins. I'll also need to map the potentiometer values from 0-512 to 255-0.

```
else{
  digitalWrite(IN1Pin, LOW);
  digitalWrite(IN2Pin, HIGH);
  MotorSpeed = map(PotVal, 0, 512, 118, 0);
  analogWrite(ENA1Pin, MotorSpeed);




  Serial.print("Pot Value: ");
  Serial.print(PotVal);
  Serial.print(" ");
  Serial.print("Reverse Motor Speed: ");
  Serial.println(MotorSpeed);
}
```

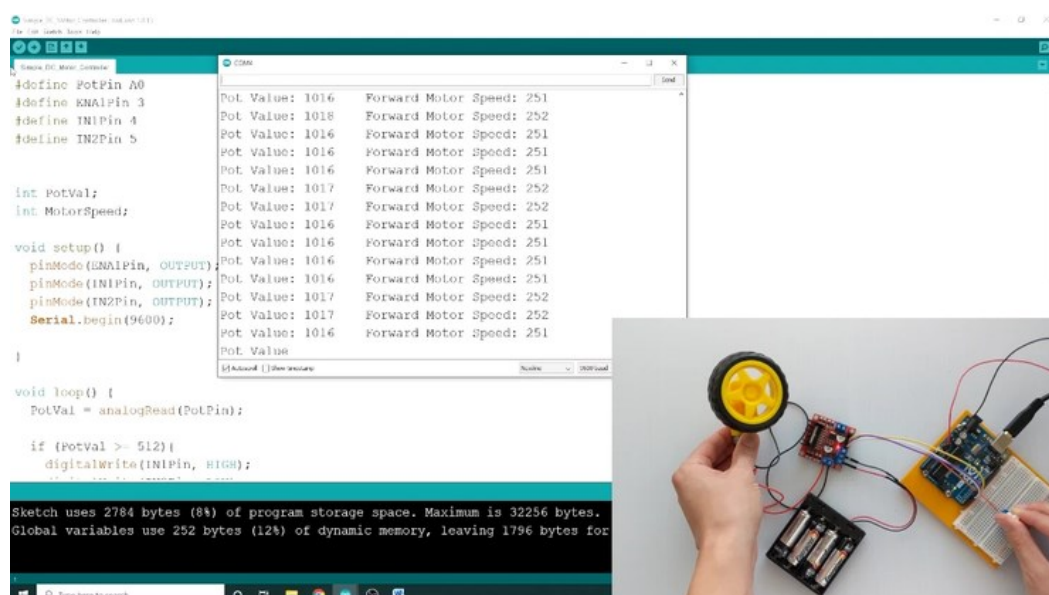The full Arduino sketch can be found [here](#). After uploading the code, rotating the potentiometer should control the speed of the motor. The motor should also spin in reverse if the potentiometer passes its midpoint.



Power Issues

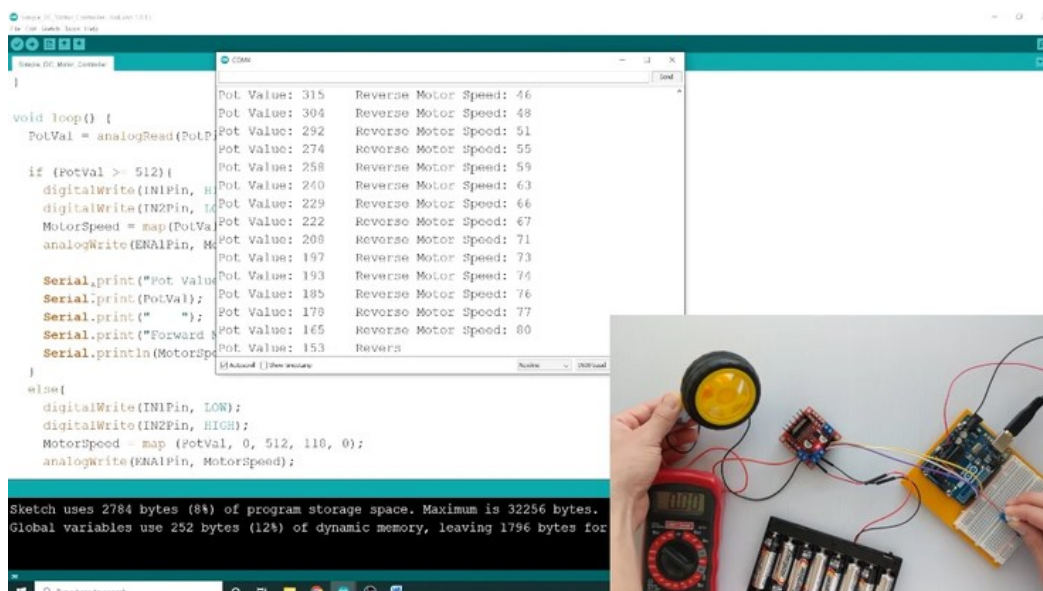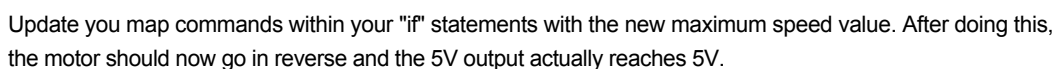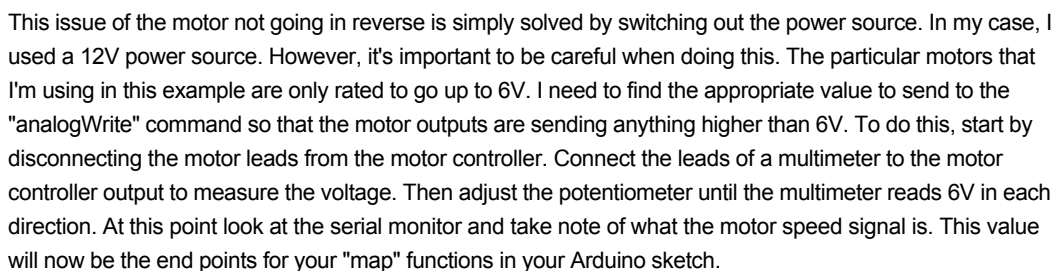If you're using a 6V power source to power this motor controller, you may encounter an issue with the motor not changing directions. You may also find that the 5V output from the motor controller doesn't actually reach 5V when the power source is at 6V.



The Bored Robot LLC is a participant in the Amazon Services LLC Associates Program, an affiliate advertising program designed to provide a means for sites to earn advertising fees by advertising and linking to Amazon.com.