















Component ✓ Free stencil ✓ Free shipping





### Introduction to DS3231 RTC Module

🖺 24 July 2020 🛔 admin 🎐 0 Comments 🕒 DS3231, DS3231 Real Time Clock, DS3231 RTC, DS3231 RTC Module, Hardware Overview, I2C RTC, Pin Configuration, Pin Diagram, Pinout, Real Time Clock Module, RTC DS3231, RTC DS3231 Module, RTC Module, Specifications

#### Share This












Hello friends! Welcome back to ElectroDuino. This blog is base on Introduction to DS3231 RTC Module. Here we will discuss Introduction to DS3231 RTC Module, module pin diagram, Hardware Overview, Specification/Features, and applications.

## Introduction

The DS3231 RTC module is a time tracking device that gives the current time and date. The word RTC is meant Real Time Clock. The RTC module made of clock chip DS3231. This module is generally used in computers, laptops, mobiles, embedded system applications devices, etc. to provide time and date. RTC module works on the I2C protocol. The module provides details such as second, minute, hour, day of the week, day of the month, month, and year including correction for leap year. One more interesting thing It can operate either in 12 Hour or in 24 Hour format. It's can be used in projects like containing data-logging, clock-building, time stamping, timers, and alarms.

## DS3231 RTC Module Pin Diagram

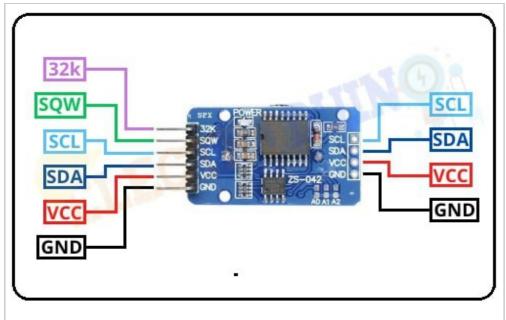


DS3231 Real Time Clock (RTC) Module Pin Diagram/Pinout/Pin Configuration

Pin Name	Description
32K	32K oscillator output. This pin outputs the stable(temperature compensated) and accurate reference clock.
SQW	The SQW pin has a cool feature, it can produce outputs one of four square-wave frequency 1 Hz, 4 kHz, 8 kHz or 32 kHz and can be possible programmatically.
SCL	This is a clock input I2C serial communication pin.
SDA	This pin is used to the data input/output for the I2C serial interface.
VCC	It is a positive power input pin of the module in range

	3.3V to 5.5V.
GND	GND is a negative(ground) power input pin

# DS3231 RTC Module Hardware Overview

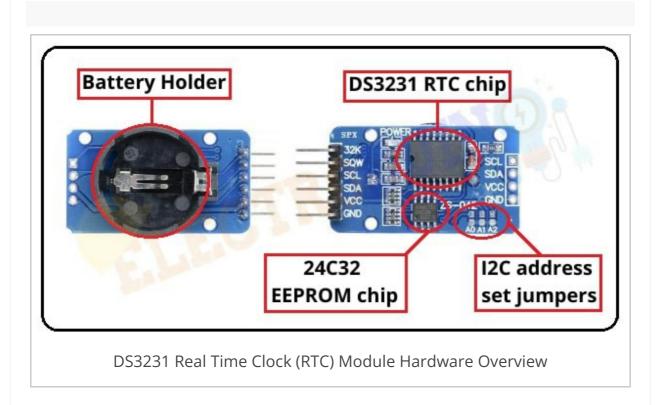

#### **Battery Holder**

The bottom side of the module has a battery holder for a 20mm 3V lithium coin cell. Any CR2032 battery can fit in the battery holder. The DS3231 incorporates a battery input and maintains accurate timekeeping when the main power to the device is interrupted.

The built-in power-sense circuit continuously monitors the status of the input (VCC) power supply to detect power failures and automatically switches to the backup supply. So, it can continue to maintain the time and date while device power is incorrect.

#### DS3231 RTC chip

The **DS3231** chip is a low-cost accurate Real Time Clock IC with communication over I2C Interface. The DS3231 is 16 pin IC, Although it

needs only 8 pins off the available 16 pins to function. The IC is operated on low power consumption when it operated on a battery then it consumes less than 500 nA power. It manages all timekeeping functions.

This Chip clock/calendar can provide seconds, minutes, hours, day, date, month, and year information. This IC clock operates in the format of either the 24-hour or 12-hour with AM/PM indicator. The end of the month date is automatically adjusted the months which has less than 31 days. It can corrections for leap years.

#### Temperature Compensated Crystal Oscillator(TCXO)

The DS3231 is driven by a 32kHz temperature compensated crystal oscillator (TCXO). It's highly immune to external temperature changes. So the external temperature can not affect the oscillation frequency of this crystal.

Temperature Compensated Crystal Oscillator(TCXO) is packaged inside the RTC chip, making the whole package bulky.

#### Temperature Sensor

Also a temperature sensor inside the IC package.

Which compensates the frequency changes by adding or removing clock ticks so that the timekeeping stays on track.

That's the reason Temperature Compensated Crystal Oscillator provides a stable and accurate reference clock and maintains the RTC to within  $\pm 2$  minutes per year accuracy.

#### 24C32 EEPROM chip

RTC module also comes with a 32 bytes Atmel 24C32 EEPROM chip which having limited read-write cycles. It can be used to save settings or clock/calendar. It uses the I2C interface for communication and shares the


same I2C bus as DS3231.

#### EEPROM I2C address set jumpers

We can be changed easily the EEPROM I2C address using the three A0, A1, and A2 solder jumpers. Each one of these is used to hardcode in the address and we can set the address by shorting the jumper in the proper way.

According to the 24C32 EEPROM chip's datasheet, these 3 bits are placed at the end of the 7-bit I2C address, just before the Read/Write bit. These 3 address inputs can take 2 states, either HIGH/LOW. So, we can create 8 (23) different combinations(addresses).

The address set by shorting the jumper,

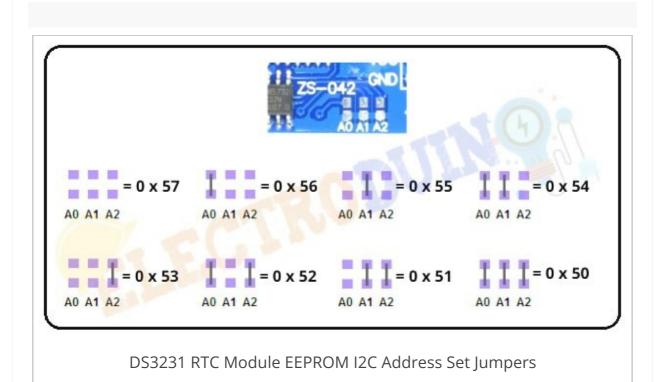

By default, all the 3 address inputs are pulled HIGH using onboard pullups, giving 24C32 a default I2C address of  $1010111_{Binary}$  or  $0x57_{Hex}$ .

#### **Module Specifications and Features**

Parameter	Value
Range of Operating Voltage	3.3V – 5V
Typical voltage supply	5V

Maximum voltage at SDA, SCL	VCC + 0.3V
Operating temperature	-45°C to +80°C
Real Time lock chip	DS3231 I2C
EEPROM Chip	AT24C32 32K I2C EEPROM memory
Configurable I2C device Address for AT24C32	Using SMD jumpers on PCB (A0, A1, A2)
I2C interface	400Khz
Battery type	LIR2032 rechargeable lithium battery
Power consumption	500nA
Digital temperature sensor accuracy	±3°C
Clock Provide	Hour, Minutes, Seconds, AM/PM.
Calendar provides	Day, Date, Month, Year.
Accuracy	+2ppm to -2ppm for 0°C to +40°C, +3.5ppm to -3.5ppm for -40°C to +85°C
PCB Size	38mm (length) * 22mm (W) * 14mm (height)

# **Application**

- To design real time clock.
- DIY projects.
- Robotics projects.
- Arduino projects.
- Raspberry-Pi projects.
- Electrical/Electronic projects.

**Share This** 











#### ← Introduction to DS1307 RTC Module


#### Dual Axis Joystick Module | How it's works →




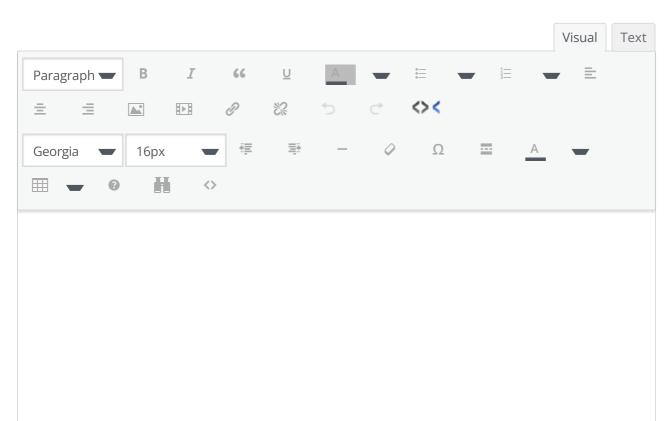
#### Leave a Reply

Your email address will not be published. Required fields are marked \*



Name *				
Email *				
Email				
Website				
☐ Save my name, email, and website in this browser for the next time I comment.	•			
Post Comment				
Tost comment				
Recent Posts				
D. A. C. V. AUSTES T. I.C.				
Rain Alarm Circuit using NE555 Timer IC				
Automatic Room Light Controller with Bidirectional Visitor Counter				
Bidirectional Visitor Counter using Arduino				
BD140 Transistor – Pinout, Specifications, Datasheet				
Interface RC522 RFID Reader with Arduino   Arduino Code				
BD139 Transistor – Pinout, Specifications, Datasheet				

## **FOLLOW US**









#### Navigation

**TUTORIALS** 

**Electronics Components** 

**PROJECTS** 

About Us

**Privacy Policy** 

Contact us

#### **SHARE POST**















ELECTRODUINO.COM is a free online platform, it provides A Better Way to **Analog Projects** 

Arduino Projects

Arduino Tutorial for Beginners

Basic

Electronics

Display Module

Pages

About Us

Contact us

**Privacy Policy** 

Learn Electronics. Electroduino
Tutorials help electronics lovers,
makers, hobbyists, and engineers to
learn and build electronics projects.
We provide complete insight and
technical details about electronic
components and project tutorials
and guides to implement projects.

Our blog tutorials related with:

Basic electronics, Analog/Digital circuit, Arduino, Robotics, Internet of Things, Home Automation, and Engineering/school projects.

Our every tutorials and project are implemented step-by-step and provide all the details of it so that is very easy to learn electronics for beginners or developers.

Home Automation Series

Integrated Circuit (IC)

Module

Motor Driver Module

Others

Sensor

Sensor / Module with Arduino

Transistor

Uncategorised

Copyright © 2022 ElectroDuino. All rights reserved. Theme: ColorMag by ThemeGrill. Powered by WordPress.







