

LM35 Temperature Sensor Pin out, Interfacing guide, Circuit Construction and Working Principals

By EG Projects




LM35 is a temperature sensor that outputs an analog signal which is proportional to the instantaneous temperature. The output voltage can easily be interpreted to obtain a temperature reading in Celsius. The advantage of lm35 over thermistor is it does not require any external calibration. The coating also protects it from self-heating. Low cost (approximately \$0.95) and greater accuracy make it popular among hobbyists, DIY circuit makers, and students. Many low-end products take advantage of low cost, greater accuracy and used LM35 in their products. Its approximately 15+ years to its first release but the sensor is still surviving and is used in any products.

LM35 Temperature sensor Features

- Calibrated Directly in Celsius (Centigrade)
- Linear + 10-mV/°C Scale Factor
- 0.5°C Ensured Accuracy (at 25°C)
- Rated for Full -55°C to 150°C Range
- Suitable for Remote Applications
- Operates from 4 V to 30 V
- Less than 60-μA Current Drain
- Low Self-Heating, 0.08°C in Still Air
- Non-Linearity Only ±¼°C Typical
- Low-Impedance Output, 0.1 Ω for 1-mA Load

LM35 Pin Out

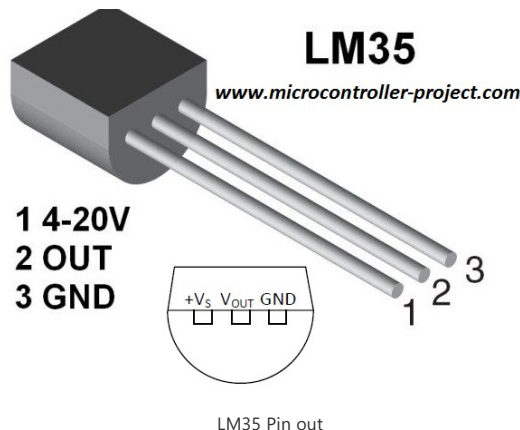

LM35 can measure from -55 degrees centigrade to 150-degree centigrade. The accuracy level is very high if operated at optimal temperature and humidity levels. The conversion of the output voltage to centigrade is also easy and straight forward.

The input voltage to LM35 can be from +4 volts to 30 volts. It consumes about 60 microamperes of current. Lm35 has many family members a few names are LM35C, LM35CA, LM35D, **LM135, LM135A, LM235, LM335**. All LM35 family members work on the same principles but temperature measuring capacity varies and also they are available in many packages (SOIC, TO-220, TO-92, TO).

LM35 Working Principle (Understanding LM35 Linear Scale Factor)

- **Linear + 10-mV/°C Scale Factor**

LM35 scale factor

In order to understand the working principle of LM35 temperature sensor we have to understand the linear scale factor. In the features of LM35 it is given to be **+10 mills volt**

per degree centigrade. It means that with increase in output of 10 mills volt by the sensor vout pin the temperature value increases by one. For example, if the sensor is outputting 100 mills volt at vout pin the temperature in centigrade will be 10-degree centigrade. The same goes for the negative temperature reading. If the sensor is outputting -100 mills volt the temperature will be -10 degrees Celsius.

LM35 temperature sensor circuit configuration

Basic Centigrade Temperature Sensor
(2°C to 150°C)

+Vs

Full-Range Centigrade Temperature Sensor

+Vs

Search this website

GO


HAVE A QUESTION?

Have a technical question about an article or other engineering questions? Check out our engineering forums EDABoard.com and Electro-Tech-Online.com where you can get those questions asked and answered by your peers!


EDA BOARD

ELECTRO-TECH-ONLINE


FEATURED TUTORIALS

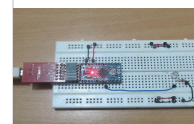

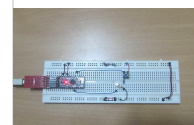
Getting Started With Arduino- (Part 1/49)



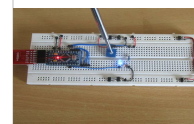
How To Use Digital Input And Digital Output Of Arduino- (Part 2/49)



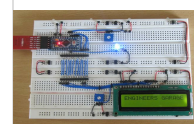How To Use Analog Input And Analog Output Of An Arduino Board- (Part 3/49)



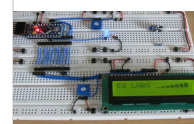
How To Interface 4 Bit LCD With Arduino- (Part 4/49)




How To Create Custom Characters On LCD Using Arduino- (Part 5/49)



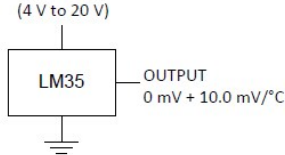Designing a Switched Mode Power Supply (SMPS)



www.microcontroller-project.com

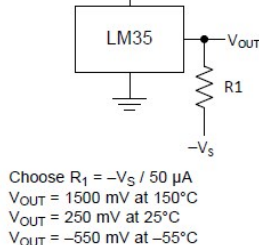

LM35 can be used in two circuit configurations. Both yield different results. In the first configuration, you can only measure the positive temperature from 2 degrees Celsius to 150 degrees Celsius. In this first configuration, we simply power lm35 and connect the output directly to analog to digital converters. In the second configuration, we can utilize all the sensor resources and can measure the full range temperature from -55 degree centigrade to 150-degree centigrade. This configuration is a little complex but yields high results. We have to connect an external resistor, in this case, to switch the level of negative voltage upwards. The external resistor value can be calculated from the formula given below the configuration circuit. The second configuration circuit can be made in various ways. To see about the second configuration circuits visit the LM35 **datasheet** by Texas Instruments. Texas Instruments **data sheet** enlists the circuit with clear component values.

Although the first configuration did not need a resistor at the output side, I recommend connecting an 80 k to 100 k resistor between vout and gnd pin. When I performed several experiments I noticed that the readings some time fluctuate and the vout pin floats. So a resistor between vout and gnd tights the vout pin low and prevents the pin from floating.

PARAMETER	VALUE
Accuracy at 25°C	±0.5°C
Accuracy from -55 °C to 150°C	±1°C
Temperature Slope	10 mV/°C

LM35 accuracy level

The accuracy parameters for both configurations are different. The average accuracy level is +- 1 degree Celsius for both configurations. But the accuracy level decreases for temperature between 2 degrees to

25-degree centigrade. Now that we have discussed the LM35 temperature sensor pinout, structure, linear scale factor and accuracy level its time to list down the steps on how to measure temperature using LM35 temperature sensor.

Steps to calculate temperature using LM35 temperature sensor

- Build circuit.
- Power LM35 vcc to +5-20 volts and gnd to ground.
- Connect Vout to analog to digital converter input.
- Sample the ADC reading, vout output voltage.
- Convert the voltage to temperature.

Formula to convert voltage to temperature

The formula to convert the voltage to centigrade temperature for LM35 is

$$\text{Centigrade Temperature} = \text{Voltage Read by ADC} / 10 \text{ mV(mills Volt)}$$

I divided by 10 mV because Linear scale factor is for LM35 is 10mV.

Following the above steps and tutorial, you can easily interface LM35 temperature sensor with any microcontroller that has a built-in analog to digital converter pins. Almost all the microcontrollers today have built-in ADC.

Some projects that are created using LM35 and different microcontrollers.

LM35 temperature monitor over wifi

LM35 measuring temperature with Arduino

LM35 measuring room temperature with 89c51 microcontroller and ADC0804

Filed Under: Electronic Projects

Tagged With: circuit, lm 35, pinout, Sensor features, temperature sensor

Questions related to this article?

STAY UP TO DATE



Sign up and receive our weekly newsletter for latest Tech articles, Electronics Projects, Tutorial series and other insightful tech content.

EE TRAINING CENTER CLASSROOMS

EE LEARNING CENTER

An online technical education portal featuring training center classrooms.

EEworld ONLINE [LEARN MORE](#)

MORE EE CLASSROOMS

RECENT ARTICLES

- How to animate text on SSD1306 using MicroPython and ESP8266
- Sensor value (data) display on TFT LCD using Arduino – Part III
- Transfer function, quality factor, and cut-off frequency
- How to read input from USB keyboard on Arduino
- Broadcom and Arista offer industry's first open, end-to-end RDMA networking solution

SUBMIT A GUEST POST

JOIN US AS A **GUEST POST WRITER**

KNOW MORE

ENGINEERS GARAGE

EDABOARD.COM DISCUSSIONS

- Continuous Current Op-Amp
- DSP Chip and Eval Board
- Multiplication of two fractional numbers

Tell Us What You Think!!

You must be logged in to post a comment.

- Dead time calculation in dual active bridge converter
- Help with PSice error

ELECTRO-TECH-ONLINE.COM DISCUSSIONS

- cordless vacuum dilemma
- computer Christmas lights
- Help With Dual Rail Power Supply
- can bus, just a question
- Purpose of rating 120MHz to the "audio" transistor?



Connect with Engineers Garage



ENGINEERS GARAGE
An EE World Online Resource

ANALOG IC TIPS
CONNECTOR TIPS
DESIGNFAST
EDABOARD FORUMS
EE WORLD ONLINE
ELECTRO-TECH-ONLINE FORUMS
MICROCONTROLLER TIPS

POWER ELECTRONIC TIPS
SENSOR TIPS
TEST AND MEASUREMENT TIPS
5G TECHNOLOGY WORLD
ABOUT US
CONTACT US
ADVERTISE