



ARTICLES

LANGUAGES ▾

PROJECTS ▾

ELECTRONICS ▾

INDUSTRIAL ▾

ENGINEERING ▾

RASPBERRY PI


AMAZON STORE ▾

SUPPORT ME

CCS C Compiler

For PIC® MCUs

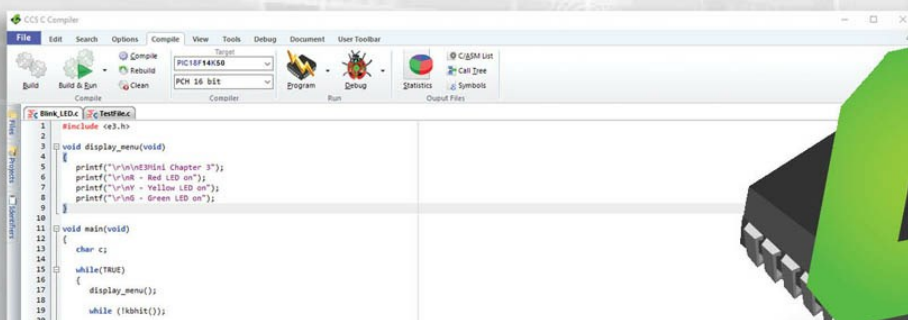Experience a pro-level C compiler paired with powerful libraries of built-in functions, ready to run program examples and PIC® MCU specific functions.



ARDUINO PROJECTS

Common Anode and Common Cathode seven segment display “Arduino project for beginners”

Engr Fahad — May 5, 2019 • add comment



(Last Updated On: April 12, 2021)



Table of Contents

- 1. Description:
 - 1.1. Amazon Links:
- 2. Common Anode & Common Cathode Displays:
 - 2.1. Types of 7 Segment display:
 - 2.2. Common Anode 7-segment display:
 - 2.3. Common Cathode 7-segment display:
- 3. Seven Segment Display Arduino Programming:
- 4. Watch Video Tutorial:

Search ...

Search

RECENT POSTS



5.8GHz FPV Camera, HD Wireless Camera with OTG Receiver for Android
January 2, 2022



DIY Racing Drone using Naze32, Puda Rooster 230, EMAX Motors 2600kv
January 2, 2022



Naze32 Quadcopter Drone PID tuning using Betaflight, How to PID Tune your Drone
December 29, 2021



Diy 12V Mini Electric Griddle, Electric Hotplate, Electric Frying Pan
December 29, 2021




How to make Arduino Laser Turret using Servo motors and Joystick
December 20, 2021



How to make Lithium Ion Battery using 3S BMS and 4S BMS
December 15, 2021



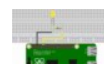ESP8266 Car Control using Android App and WiFi
December 15, 2021



How to use led with Arduino and Raspberry pi, for beginners
December 14, 2021



VB.Net Tutorial: Buttons, Labels and TextBox using Visual Basic
December 14, 2021



Diy battery Spot Welding Machine, Homemade Spot Welder with automatic circuit
December 12, 2021

BITTELE
 Turn-Key PCB Assembly

- Better price
- Complete turnkey quote in minutes
- Faster order processing
- Automated BOM optimization
- Online order tracking

ORDER NOW!

Description:

Common Anode and Common Cathode Seven segment display

In this tutorial, you will learn how to use a seven segment display with Arduino Uno. Common Anode and common cathode type seven segment displays are widely used in electronic meter, Temperature display system, RPM monitoring gadgets, digital clocks, and other electronic devices that display numerical information. Due to its popularity, I decided to make a very detailed tutorial on how to use the common Anode and common Cathode seven segments with Arduino.

Amazon Links:

[12v Adaptor:](#)

[Arduino Uno](#)

[Arduino Nano](#)

[Mega 2560:](#)

[seven segments common anode:](#)

[seven segment common cathode:](#)

Other Tools and Components:

[Top Arduino Sensors:](#)

[Super Starter kit for Beginners](#)

[Digital Oscilloscopes](#)

[Variable Supply](#)

[Digital Multimeter](#)


[Soldering iron kits](#)

[PCB small portable drill machines](#)

**Please Note: These are affiliate links. I may make a commission if you buy the components through these links. I would appreciate your support in this way!*

Common Anode & Common Cathode Displays:

Seven Segment Display

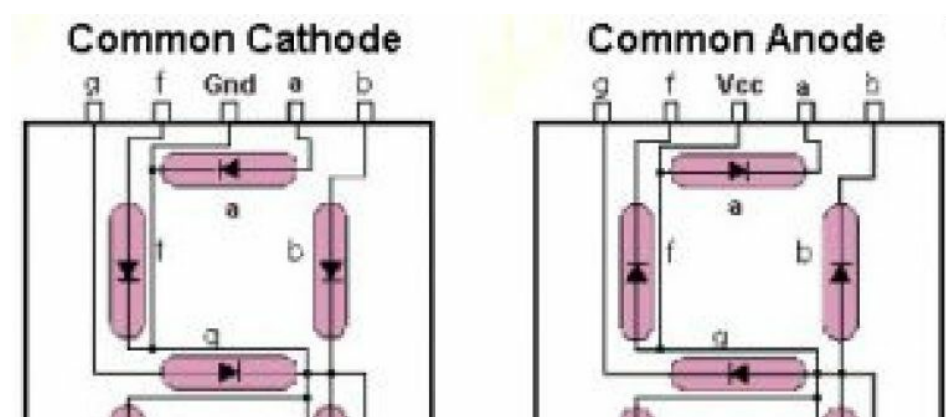

RECENT COMMENTS

miniduos on Arduino Oled i2c Display 128×64 with examples, Wiring, and Libraries issues solved

Bertran on NRF24L01 with Arduino, NRF24L01 Pinout, and Example Codes

pola .akhila on Pointer Arithmetic in C++ with Programming Examples

yonas on Soil NPK Sensor with Arduino and Android Cell Phone Application for monitoring Soil Nutrient

Timr on Raspberry Pi 16×2 LCD I2C Interfacing and Python Programming

ARCHIVES

January 2022 (2)

December 2021 (17)

November 2021 (11)

October 2021 (11)

September 2021 (11)


August 2021 (16)

July 2021 (14)

June 2021 (14)

May 2021 (23)

April 2021 (39)

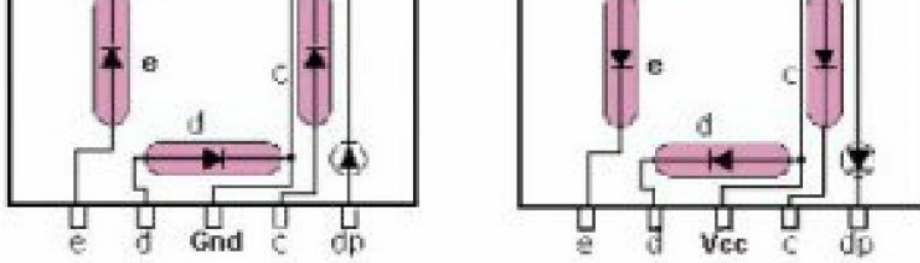

As you can see in the picture above, the pinout of both the 7 segments is exactly the same, the only difference between the two displays, is in the connection of the leds. These are called 7 “seven” segment displays because both the displays consist of 7 led’s, each segment which is an led is labeled the English letters...

A

B

C

D

E

AND

F


By turning ON and turning OFF each segment or led we can make different symbols or numbers from 0 to 9 and some English letters.

Types of 7 Segment display:

There are mainly two types of seven segment displays

- Common Anode seven segment display
- Common Cathode seven segment display

Common Anode 7-segment display:

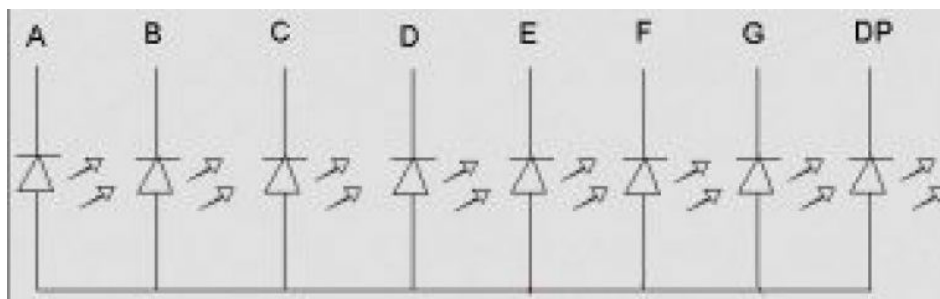

in common anode type 7-segment display, the anode side of all the led’s or segments are connected together and are connected to the desired voltage. During the practical connections, current limiting resistors are connected in series with each led if needed. Then each led or segment can be easily turned ON by applying logic 0 or low signal through a current limiting resistor to the cathode of any particular led or segment. So, for a common anode type seven segment

0 means ON

1 means OFF

March 2021 (58)

February 2021 (26)

January 2021 (35)

December 2020 (28)

November 2020 (123)

October 2020 (30)

September 2020 (23)

August 2020 (26)

July 2020 (17)

June 2020 (20)

May 2020 (25)

April 2020 (27)

March 2020 (22)

February 2020 (20)

January 2020 (13)

December 2019 (11)

November 2019 (9)

October 2019 (16)

September 2019 (15)

August 2019 (22)

July 2019 (43)

June 2019 (10)

May 2019 (52)

April 2019 (20)

CATEGORIES

Advance Electronics (29)

Advance Projects (131)

android app development (13)

Arduino + Image Processing (8)

Arduino + vb.net Projects (10)

Arduino Industrial Projects (12)

Arduino Projects (219)

Arduino Robotic Projects (8)

Arduino Wireless Projects (51)

Articles (53)

ATtinny85 (1)

Basic Electronics (108)

C sharp (C#) (15)

C++ Programming (62)

computer (6)

dc machines and batteries (7)

Digital Electronics (12)


Electric Vehicle Projects (6)

Electrical (36)

Electronics (32)

Engineering (8)


Common Cathode 7-segment display:

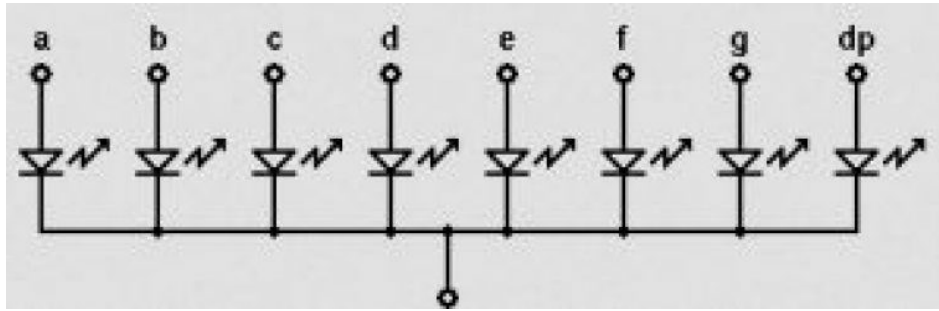


In common cathode type 7-segment display, the cathode side of all the led's or segments are connected together to logic 0 or ground. Then each led or segment can be turned ON by applying log 1 or a high signal through a current limiting resistor to the anode of particular led or segment.



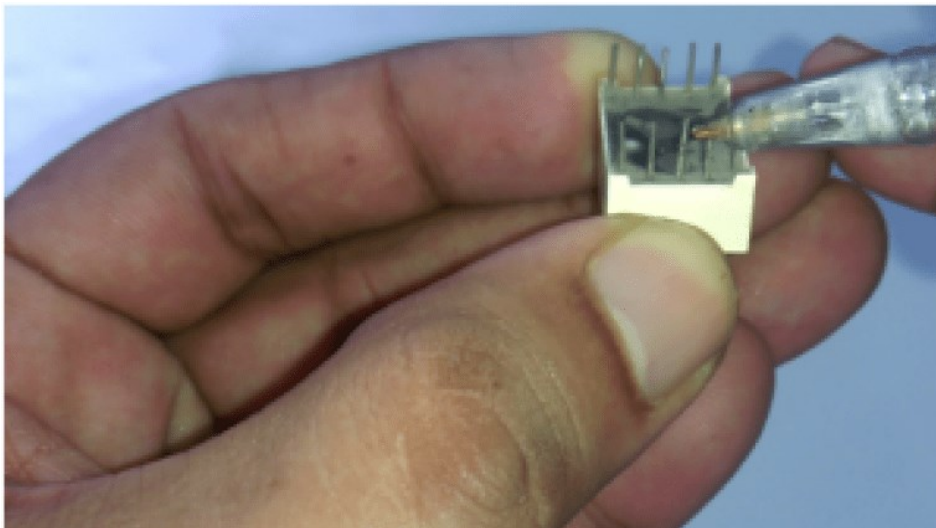Depending on the decimal digit to be displayed, the particular set of LEDs is turned on or forward biased. For example, to display the numerical digit o “Zero”, we will need to light up six of the LED segments corresponding to a, b, c, d, e, and f. this way digits from 0 to 9 can be displayed on Common Anode or Common Cathode type seven segments display.



Each seven segment display has a total of 10 pins, 5 pins on the upper side and 5 pins on the bottom side. The middle pins of both the seven segments are internally connected and can be connected with a 5v or GND depending on the type of seven segment display. If it's a common anode type then this pin will be connected with 5v or else it will be connected with the ground if this is common cathode type seven segment display.

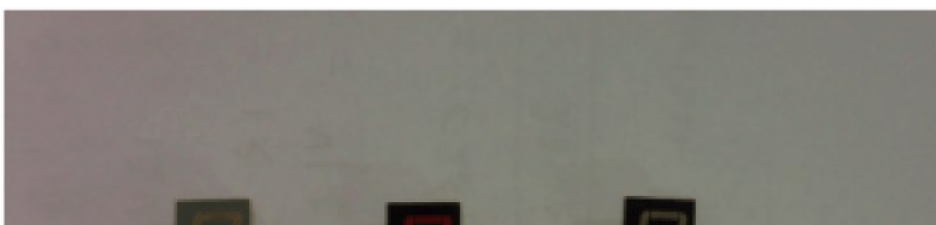

esp32 iot projects (28)

Html and CSS (8)

Industrial (5)

IOT Projects (99)

Java Programming (17)

JavaScript (16)

Matlab (16)

PHP (6)

PLC and Scada Projects (2)

PLC Projects (9)

Power Electronics (6)

Power Generation (17)

Power Projects (5)

Python Programming (38)

raspberry pi (46)

RC Plane (12)


RC Projects (8)

Simple Projects (61)

STM32 (5)

Telecommunication (11)

Vb.net programming (1)

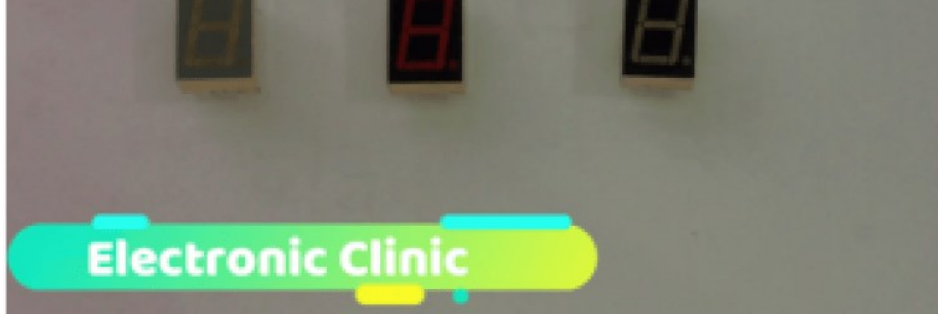

only by looking at the seven segment display it's hard to tell whether this is a common anode or common cathode type. Before we can apply the voltage lets first calculate the value of a resistor


Normally for a standard red colored seven segment display, each leg “light emitting diode” segment can draw around 15 mA to illuminate correctly; so as we are planning to use this seven segment display with the Arduino Uno, the value of the current limiting resistor would be about 200Ω.

$$(5v - 2v)/15mA,$$


Or


220Ω to the nearest higher preferred value but currently I have a 330-ohm resistor available so I will use this one. First, let's check this for the common anode type seven segment display.

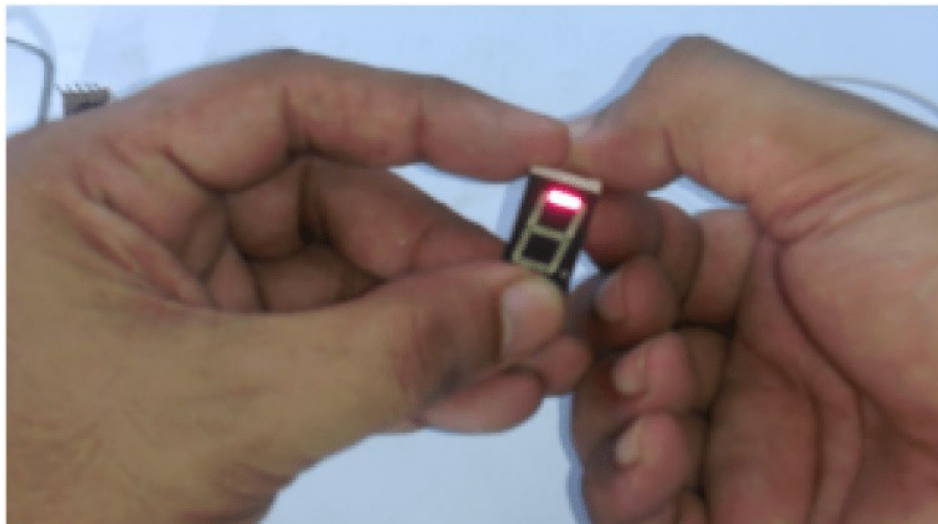Connect 5v from the Arduino with the common pin of the seven segment. now connect a 330-ohm resistor with a wire, connect one side with the Arduino GND and connect the other side of the wire with any pin of the seven segment. As you can see the led or segment can turn on so it means this seven segment is common anode type.



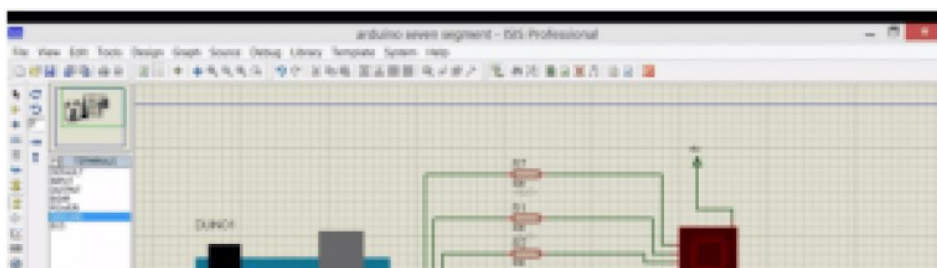we have covered all the basics now its time to use this seven segment with Arduino Uno. Before you start the practical connections I highly recommend, first you should make a Proteus simulation and understand the basics.



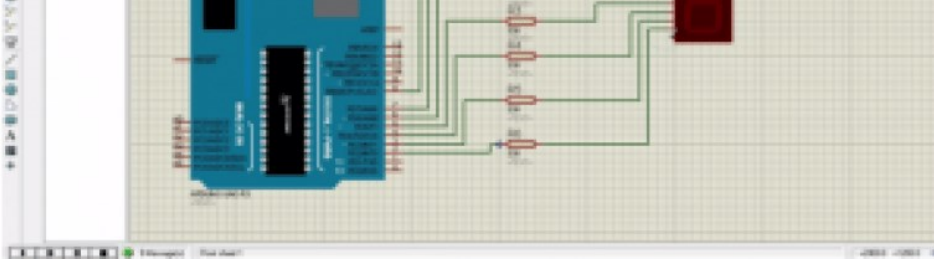

while Proteus is open, click on the pick from libraries button and search for Arduino, double click to add, now click the mouse left button to add Arduino and then select the Arduino, right click and select rotate. again click on pick from libraries button and search for common anode type seven segment, look for the common anode type seven segment and double click or click ok to add it to the list. again click on the pick from libraries button write resistor, select the resistor and click ok to add it to the list. Now add seven resistors and change their values from 10k to 330 ohm. now connect these resistor with pin2...3....4....5....6....7 ...and 8. connect 5 volts with the common of seven segment. connect pin8 of the Arduino to pina of the seven segment, similarly connect pin7 of the Arduino to pinb of the seven-segment and so on after the connections are completed now its time to start the Arduino programming.


Seven Segment Display Arduino Programming:



Common Anode and Common Cathode 7 segment display

```

1  int pina = 8;
2  int pinb = 7;
3  int pinc = 6;
4  int pind = 5;
5  int pine = 4;
6  int pinf = 3;
7  int ping = 2;
8
9  void setup()
10 {
11     pinMode(pina, OUTPUT);
12     pinMode(pinb, OUTPUT);
13     pinMode(pinc, OUTPUT);
14     pinMode(pind, OUTPUT);
15     pinMode(pine, OUTPUT);
16     pinMode(pinf, OUTPUT);
17     pinMode(ping, OUTPUT);
18 }
19
20 }
21
22 void loop()
23 {
24     // for zero
25
26     digitalWrite(pina, LOW);
27     digitalWrite(pinb, LOW);
28     digitalWrite(pinc, LOW);
29     digitalWrite(pind, LOW);
30     digitalWrite(pine, LOW);
31     digitalWrite(pinf, LOW);
32     digitalWrite(ping, HIGH);
33     delay(1000);
34     digitalWrite(pina, HIGH);
35     digitalWrite(pinb, LOW);
36     digitalWrite(pinc, LOW);
37     digitalWrite(pind, HIGH);
38     digitalWrite(pine, HIGH);
39     digitalWrite(pinf, HIGH);
40     digitalWrite(ping, HIGH);
41     delay(1000);
42
43     digitalWrite(pina, LOW);
44     digitalWrite(pinb, LOW);
45     digitalWrite(pinc, HIGH);
46     digitalWrite(pind, LOW);
47     digitalWrite(pine, LOW);
48     digitalWrite(pinf, HIGH);
49     digitalWrite(ping, LOW);
50     delay(1000);
51 }
52

```

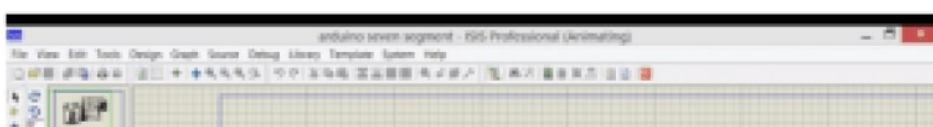

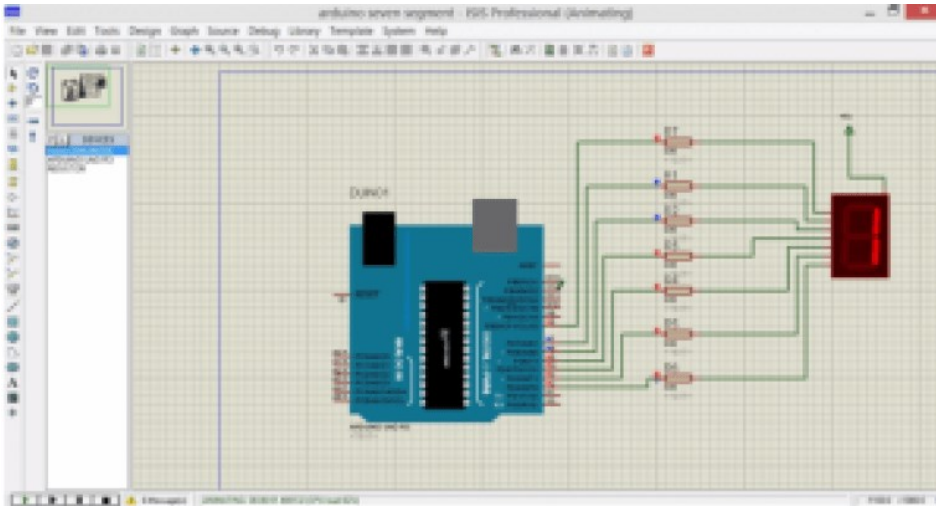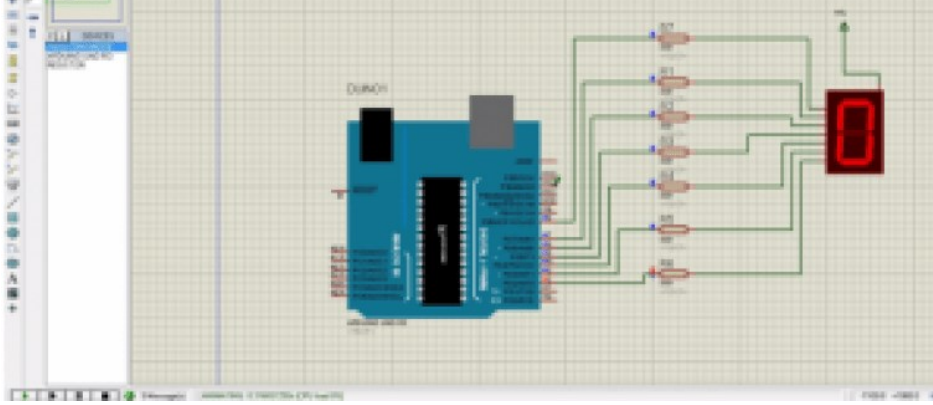

Watch Video Tutorial:



Share this:




Like this:


Loading...

- 7 segment
- 7 segment display arduino
- arduino
- arduino advanced projects
- arduino basic projects
- arduino common anode 7 segment
- arduino common anode and common cathode
- arduino programming
- arduino programming for beginners
- arduino project
- arduino project for beginners
- arduino projects
- arduino projects for beginners
- arduino simple projects
- arduino uno
- best diy website
- common anode
- common anode 7 segment display
- common anode and common cathode 7 segment display
- common cathode


Recommended For You




Diy 12V Mini Electric Griddle, Electric Hotplate, Electric Frying Pan



ESP8266 Car Control using Android App and WiFi



Kaiweets Smart Digital Multimeter Model KM601 review and how to use it



12V DC Heater Plate 80W, PTC Heater Plate, 12v solar heater

About the Author: [Engr Fahad](#)

My name is Shahzada Fahad and I am an Electrical Engineer. I have been doing Job in UAE as a site engineer in an Electrical Construction Company. Currently, I am running my own YouTube channel "Electronic Clinic", and managing this Website. My Hobbies are * Watching Movies * Music * Martial Arts * Photography * Travelling * Make Sketches and so on...

Leave a Reply

Enter your comment here...

Subscribe for Updates






Enter your email address to subscribe to this blog and receive notifications of new posts by email.

Email Address

Subscribe

Follow Us

Stay updated via social channels

About Us

“**Electronic Clinic**” is an Electrical and Electronics Engineering community built and run by professional electrical engineers and computer experts. We share Electrical, Electronics, Power, Robotics, Software, Communication, IOT “Internet Of Things”, GSM, Industrial and communication projects. Thus helping students and professionals with their projects and work. We also offer innovative ideas and solutions.